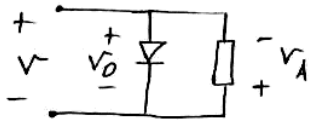



پاسخنامه تشریحی تمرین سری چهارم مبانی مدارهای الکتریکی و الکترونیکی

نویسنده: محمدعلی پشنج


پاسخ سوال ۱: بلایرته‌ی دیود و عنصر A، عکس یکدیگر است. لذا،


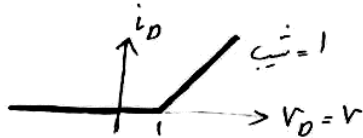
$$v = v_D, \quad \boxed{v = -v_A} \Rightarrow \boxed{v_A = -v}$$




« شکل ۱ »

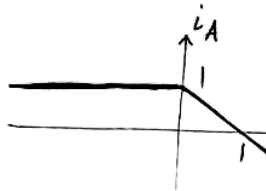

$$\Rightarrow i_A = \begin{cases} -v_A + 1 & v_A > 0 \\ 1 & v_A < 0 \end{cases}$$




$$\boxed{v_A = -v} \Rightarrow$$
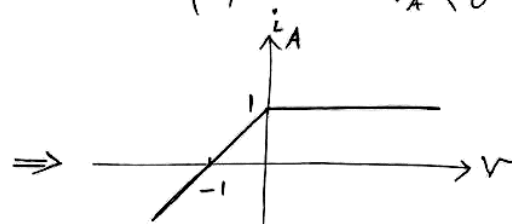
$$i_A = \begin{cases} v + 1 & v < 0 \\ 1 & v > 0 \end{cases}$$



« شکل ۲ »


شکل های ۱ و ۲ را جمع می کنیم

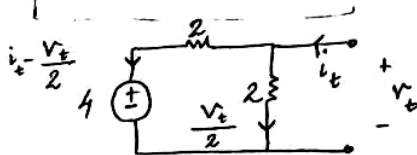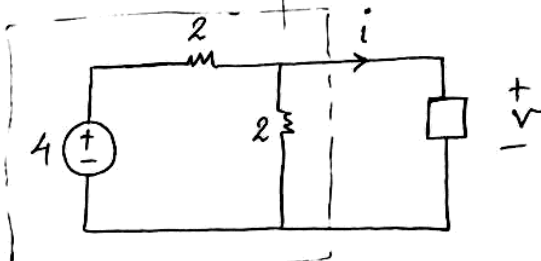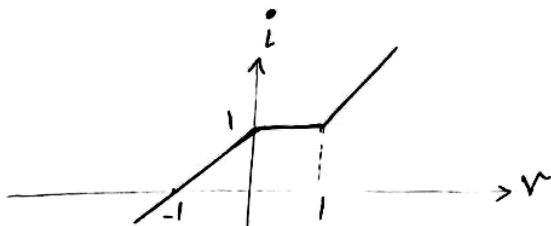


معادل بست می آوریم:

$$KVL) 2(i_t - \frac{v_t}{2}) + 4 - v_t = 0 \Rightarrow \boxed{v_t = i_t + 2}$$
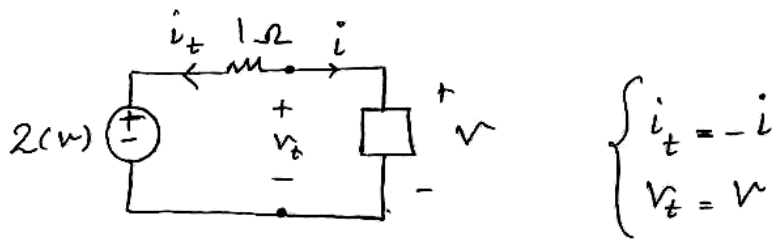
$$\Rightarrow V_t = i_t + 2 \quad (*) \Rightarrow R_{th} = 1 \Omega \quad V_{th} = 2 \text{ (V)}$$



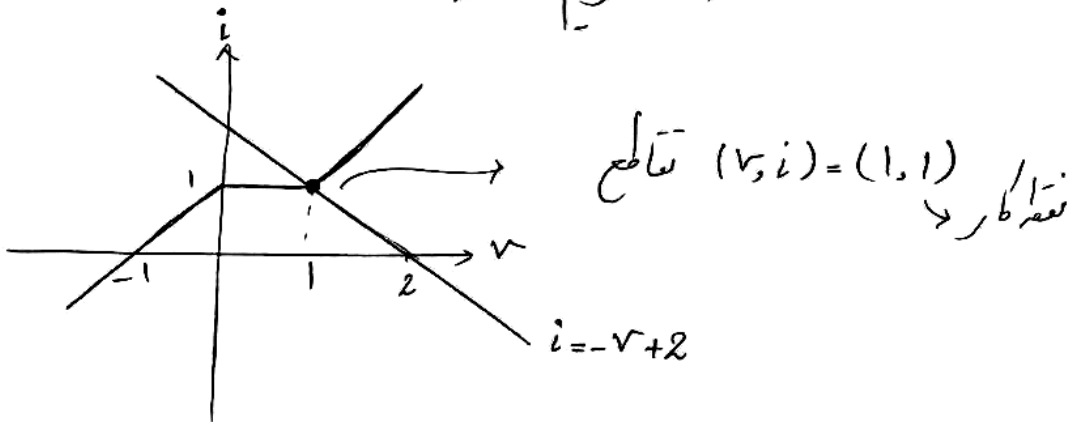
$$(*) \Rightarrow V = -i + 2 \Rightarrow \text{رسم} \Rightarrow i = -V + 2$$



$$V = 1 \Rightarrow V_D = V = 1 \Rightarrow (i_D - V_D) \text{ منفی} \Rightarrow i_D = 0$$

$$P_D = V_D i_D = (1)(0) = 0 \text{ W}$$

پاسخ سوال ۲:

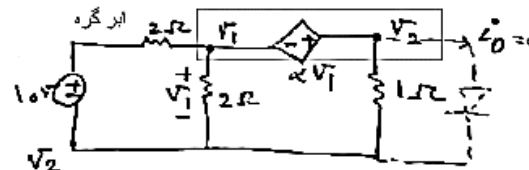

$$\frac{V_1 - 10}{2} + \frac{V_1}{2} + \frac{(\alpha + 1)V_1}{1} = 0 \quad V_1 = \frac{5}{\alpha + 2}$$

برای ولتاژ V_2 باید متغیر باشد، جریان از آن عبور نمی‌کند $V_2 \leq 0$

$$V_2 = V_1 + \alpha V_1 \leq 0 \rightarrow \frac{5(\alpha + 1)}{(\alpha + 2)} \leq 0 \rightarrow -2 < \alpha \leq -1$$

پاسخ سوال ۳:

First, let us show that D_1 on $\Rightarrow D_2$ off, and D_2 on $\Rightarrow D_1$ off.

Consider D_1 to be on $\rightarrow V_{AB} = 0.7 + 1 + i_1 R_1$.

Note that $i_1 > 0$, since D_1 can only conduct in the forward direction.

$\Rightarrow V_{AB} > 1.7 \text{ V} \Rightarrow D_2$ cannot conduct.

Similarly, if D_2 is on, $V_{BA} > 0.7 \text{ V}$, i.e., $V_{AB} < -0.7 \text{ V} \Rightarrow D_1$ cannot conduct.

Clearly, D_1 on $\Rightarrow D_2$ off, and D_2 on $\Rightarrow D_1$ off.

- * For $-0.7 \text{ V} < V_i < 1.7 \text{ V}$, both D_1 and D_2 are off.
 \rightarrow no drop across R , and $V_o = V_i$. (1)

- * For $V_i < -0.7 \text{ V}$, D_2 conducts. $\rightarrow V_o = -0.7 - i_2 R_2$.
 Use KVL to get i_2 : $V_i + i_2 R_2 + 0.7 + R i_2 = 0$.

$$\rightarrow i_2 = -\frac{V_i + 0.7}{R + R_2}, \text{ and}$$



$$V_o = -0.7 - R_2 i_2 = \frac{R_2}{R + R_2} V_i - 0.7 \frac{R}{R + R_2}. \quad (2)$$

- * For $V_i > 1.7 \text{ V}$, D_1 conducts. $\rightarrow V_o = 0.7 + 1 + i_1 R_1$.
 Use KVL to get i_1 : $-V_i + i_1 R + 0.7 + 1 + i_1 R_1 = 0$.

$$\rightarrow i_1 = \frac{V_i - 1.7}{R + R_1}, \text{ and}$$


$$V_o = 1.7 + R_1 i_1 = \frac{R_1}{R + R_1} V_i + 1.7 \frac{R}{R + R_1}. \quad (3)$$

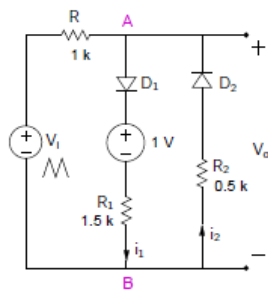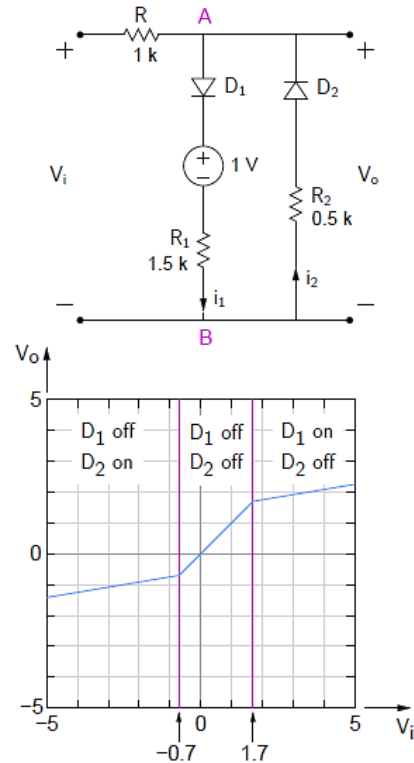
- * Using Eqs. (1)-(3), we plot V_o versus V_i .



Point-by-point construction of V_o versus t :

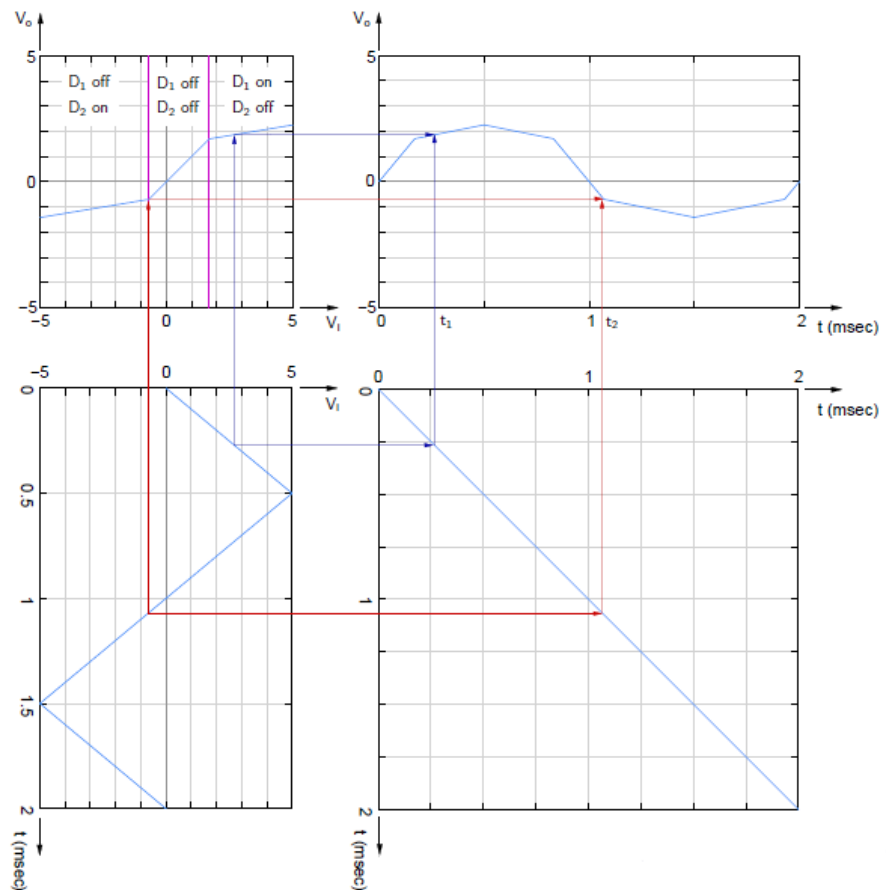Two time points, t_1 and t_2 , are shown as examples.



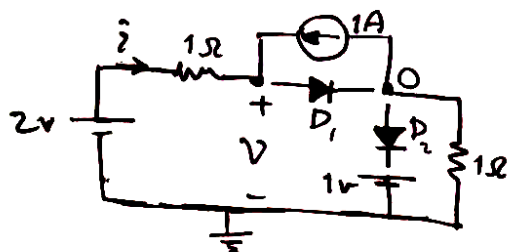

ابتدا فرض می‌کنیم هر دو دیود قطع هستند:


$$i_{D1} = i_{D2} = 0 \Rightarrow i = -1A$$

$$V = +2 - i = 2 - (-1) = 3V$$

$$V_O = 0 + 1 \times i = -1V$$

$$\Delta V_{D1} = V - V_O = 3 - (-1) = 4V \gg 0$$

برای مدار داریم

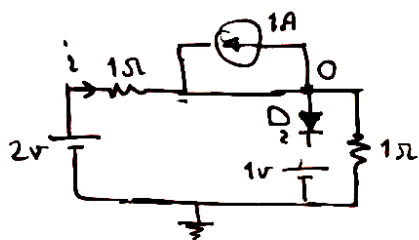

$\Rightarrow D_1$ روشن است

$$\frac{V_O - 0}{1} + \frac{V_O - 2}{1} = 0 \Rightarrow V_O = 1V$$



$$\Delta V_{D2} = V_O - 1 = 0V \geq 0$$

$\Leftarrow D_2$ هم وصل است.


$$i = \frac{2 - 1}{1} = 1$$

$$i = 1$$

$$V = 2 - 1 \times i = 2 - 1 = 1V$$


$$V = 1V$$

پس مدار این چنین می‌شود.

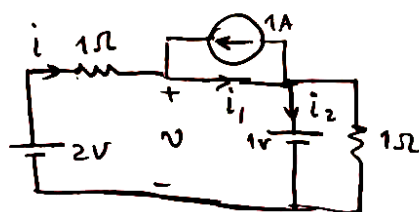

پاسخ سؤال 5 :


ابتدا فرض می‌کنیم هر دو دیود قطع هستند :

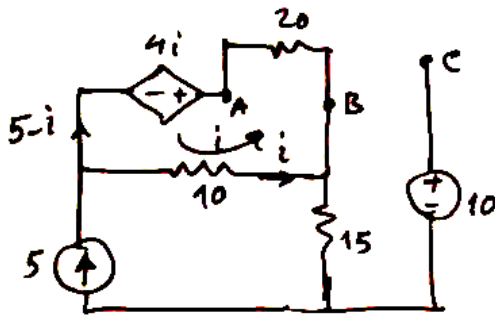

$$-10i + 20(5-i) - 4i = 0$$

$$\Rightarrow -34i = -100 \rightarrow i = \frac{100}{34} = \frac{50}{17}$$
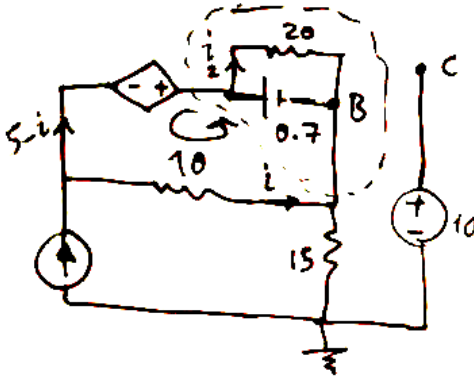
$$\Rightarrow V_A - 20(5-i) = V_B \rightarrow V_A - V_B = 20(5 - \frac{50}{17}) \approx 41.18 \text{ V}$$



← پس دیودین A و B وصل است .

چون $41.18 > 0.7$

$$i_2 = \frac{0.7}{20}$$


$$-10i + 0.7 - 4i = 0 \rightarrow 0.7 = 14i$$

$$i = \frac{0.1}{2} = \frac{1}{20}$$

KCL : $\frac{V_B - 0}{15} + (-i) + (-(5-i)) = 0 \rightarrow \frac{V_B}{15} = 5 \rightarrow V_B = 75 \text{ V}$

$$V_C = 0 + 10 = 10 \rightarrow V_B - V_C = 75 - 10 = 65 \text{ V} > 0.7 \text{ V}$$

پس دیودین B و C نیز وصل است :

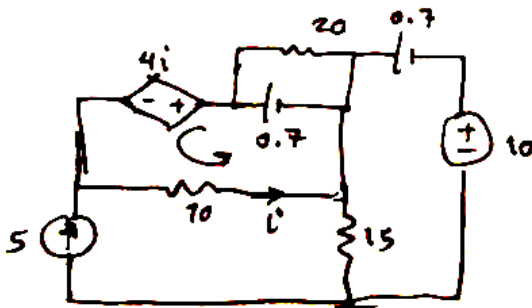

$$\text{KVL : } -10i + 0.7 - 4i = 0$$

$$i = \frac{1}{20} \text{ A}$$